

Connect the car



Read the named terminals here; page 2 locates the actual solder pads. All grounds connect together. Crossings connect only where marked with a dot.

1 BATTERY




2S / 7.4 V / 300 mAh
8.4 V when fully charged

XT30
unplug = OFF

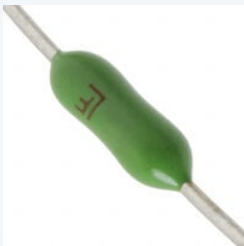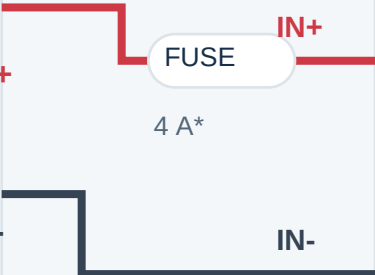

Fuse family photo
[Details: page 6](#)

2 YOUR LARGE BUCK

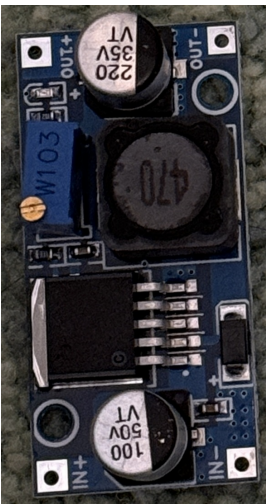

Adjust output to 5.00 V

OUT+ / 5 V BUS

OUT- / GND BUS

3 FRONT-LEFT SERVO




Owned continuous-rotation unit

4 REAR-RIGHT SERVO



Same supply; separate signal

5 LOLIN S2 MINI

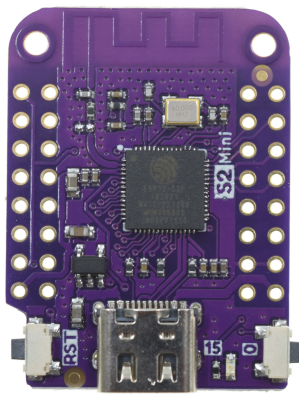

USB unplugged while driving

VBUS
GND

J_PWR
JP

RED +
BROWN -
S

GPIO18 > RIGHT

GPIO16 > LEFT SIGNAL

At the 5 V / GND split

Add **220 uF / 10 V electrolytic** (+ to 5 V; striped negative to GND), plus **100 nF ceramic** across the same rails. Keep leads short. Preserve the buck's onboard capacitor.

Battery sensing: included on page 4


The existing receiver firmware also needs **GPIO3 + GPIO7** and the switched divider. It stops motion at 7.0 V; it does **not** disconnect the pack. Unplug after stopping.

* Fuse rating is provisional. Photos show reference servos; wire functions, not plug orientation, define the connections.

Exactly where each wire lands


Component side facing you. S2 antenna at the top; USB-C at the bottom. Photos are not mirrored.

LOLIN S2 MINI v1.0.0 REFERENCE

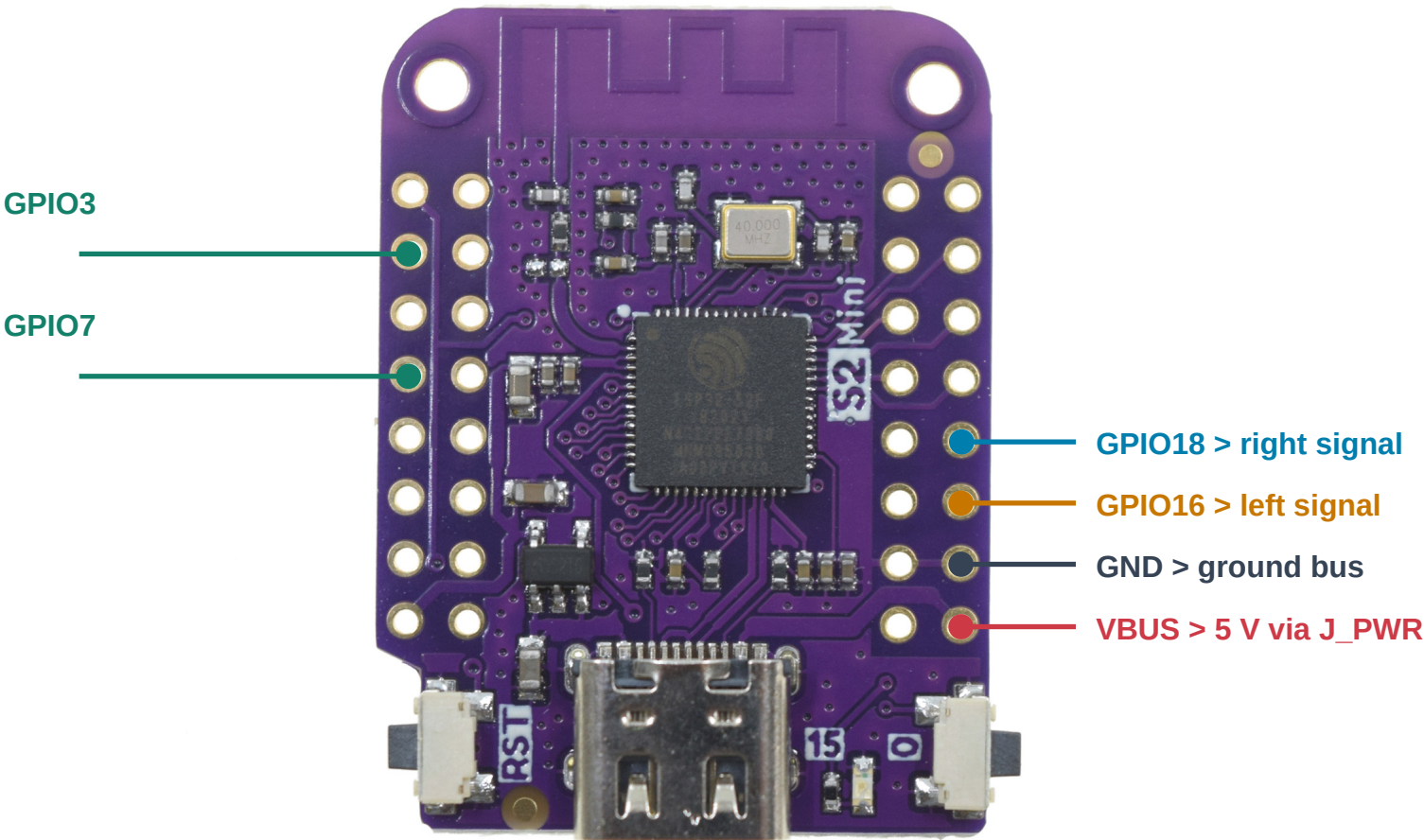

Left GPIO3 / GPIO7: sensing only (page 4)
Use GPIO labels. Inner-row GPIO17 is NOT the right servo pin.

YOUR LARGE BUCK: SAME ORIENTATION

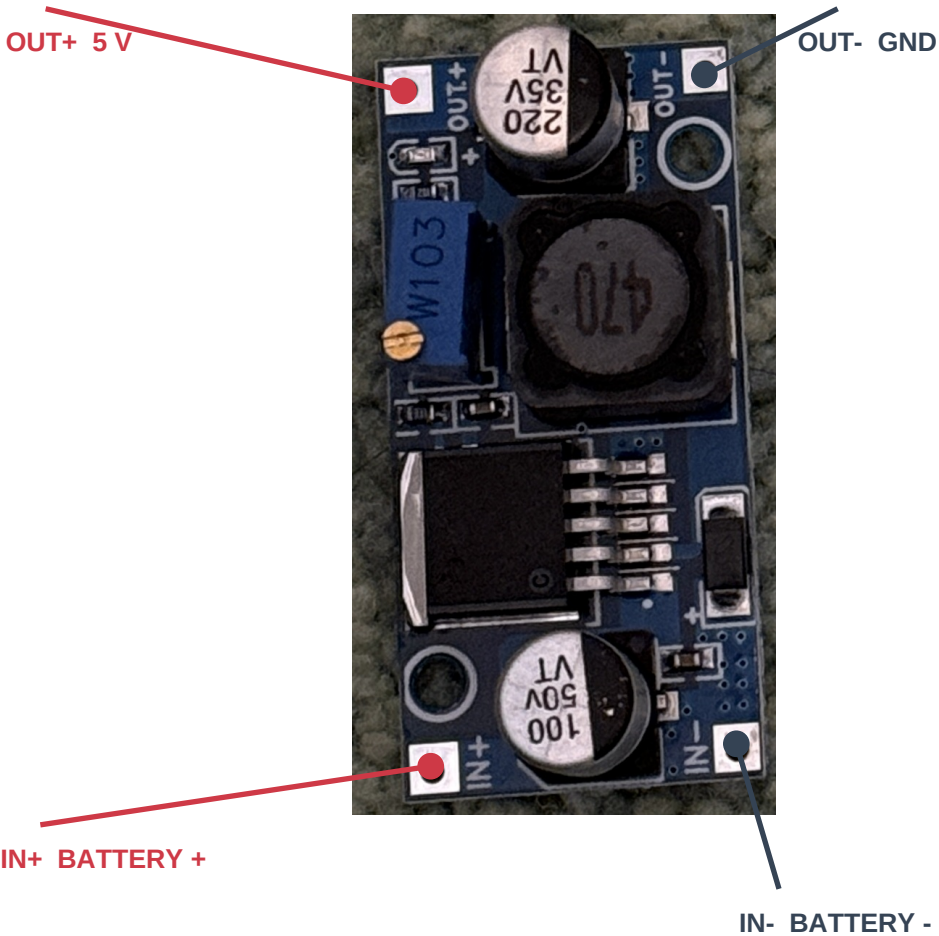

Blue trimmer sets output. Measure OUT+ to OUT- and set **5.00 V with all loads disconnected**. IC marking is not readable: confirm the board type.

Soldered wiring + removable connectors

Bare S2 holes and converter pads need soldered wires or soldered headers. Use 22 AWG or thicker for the battery and main 5 V / GND paths. Servo red normally means supply; brown/black ground; orange/yellow signal. Verify your servo wires before fitting a 3-pin extension. Split its three wires to the correct nets - do not plug the whole servo lead onto random adjacent S2 pins.

Battery, plug and converter choice

Reuse the larger buck for this prototype. A custom power PCB is not required.



BUY: LUMENIER 300

2S 75C LiPo, XT30

48 x 17 x 12 mm
18 g; 7.4 V nominal
8.4 V fully charged

\$13.49; listed available
at the research snapshot.



YOUR YELLOW CONNECTORS

The photo establishes the XT family, but does not distinguish **XT30** from **XT60**. Read the molded marking.


XT30: use the mating harness half.
XT60: buy an XT30 mating pigtail; a bulky adapter also works but increases footprint.

Check + / - with a meter. Housing shape or wire color alone is not proof of polarity.

[RaceDayQuads product / purchase page](#)

Why the large buck wins here

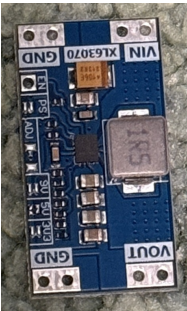A 2S pack feeds a step-down converter naturally. Allowing 1.2 A per servo plus 0.4 A for the S2 gives a **provisional 2.8 A at 5 V**. Actual servo peaks are unknown. The LM2596 IC is rated 3 A with suitable parts and cooling; this particular board must still pass load and temperature checks at 8.4 V and 7.0 V.



Why not the small XL63070 board?


It appears to be a TPS63070-style buck-boost module; the IC is unconfirmed. TI specifies 2 A output at 4 V in / 5 V out. That is below our provisional load. A 1S design at 14 W could also need about 5 A near 3.3 V. Smaller hardware needs current measurements first.

Battery handling and fit

12 mm is the pack thickness, not a promised installed height: leave room for padding and lead bends. This hobby pack has no verified protection PCB. Neither owned converter provides charging, balancing or a suitable LiPo cutoff. Use a 2S balance charger and unplug the pack after each run.

Battery sensing for the existing firmware

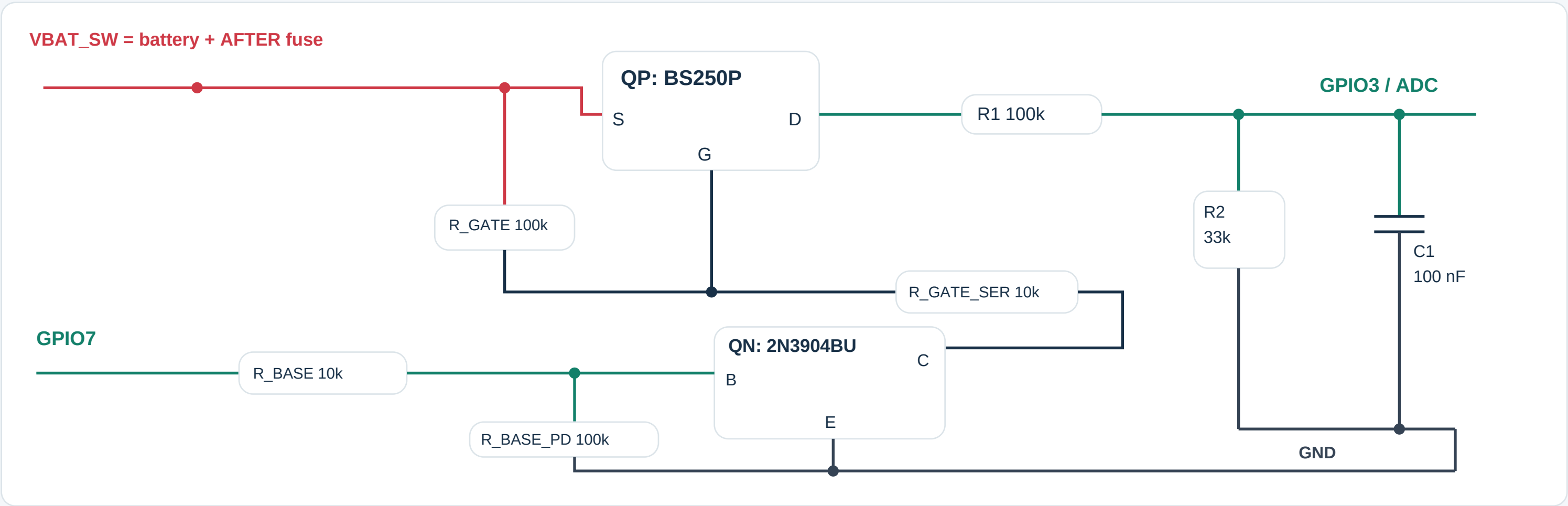A small insulated perfboard carries these low-current parts; motor current stays in the main harness.



Parts and terminal identification

QP: Diodes BS250P P-channel MOSFET: source to raw fused battery, drain to R1, gate to the resistor network shown.

QN: onsemi 2N3904BU NPN: emitter to GND, collector to R_GATE_SER, base to R_BASE.

Resistors: 3 x 100k, 2 x 10k, and 1 x 33k; use 1% for R1/R2. C1: 100 nF ceramic, 16 V or higher.

Match the exact maker's package-view drawing before soldering; transistor terminal letters are not left-to-right lead positions.

What it does - and what it cannot do

GPIO7 HIGH enables sensing; wait at least 20 ms before sampling GPIO3. Return GPIO7 LOW afterward.

8.4 V pack = about 2.084 V at GPIO3.

The switching stage avoids a sustained battery-fed ADC path when the S2 is off; do not replace it with a permanently connected divider.

Existing firmware needs pairing, servo-neutral and battery calibration before arming. Its 7.0 V stop only commands neutral. Pack voltage does not reveal an individually weak cell; monitor both cells and unplug promptly.

Build, check and use

No custom PCB. This is a soldered prototype harness, not a tested plug-and-play electrical assembly.

Wire and check in this order

1. Battery unplugged: solder the mating XT30 lead through a provisional 4 A inline fuse to IN+; negative to IN-. Insulate every joint.
2. Leave all loads disconnected. Power the buck, read OUT+ to OUT- with a multimeter and adjust to 5.00 V. Unplug before adding wires.
3. Split OUT+ and OUT- into separate servo and S2 branches. Add the capacitors. Fit J_PWR as a removable insulated connector in the S2 VBUS feed.
4. Add the page 4 sensing circuit. Check the ADC voltage and off-state behavior before connecting GPIO3. Calibrate against a meter.
5. With wheels lifted, test each servo, then both together. Check 5 V stability, resets and board temperature at 8.4 V and 7.0 V input. Do not hold a servo stalled.
6. Verify neutral on signal loss and the calibrated 7.0 V stop. Test voltage thresholds with an adjustable supply, not by deeply discharging the battery.

Before connecting USB to the S2

Unplug the battery, remove J_PWR, and disconnect both servo signal wires. Ground may remain connected. The S2 VBUS header is connected to USB power: battery disconnection alone can still let USB feed the servos or buck backward through the 5 V wire. Restore J_PWR and signals only after USB is removed.

Charge outside the car

Use a **2S LiPo balance charger** set for 4.20 V/cell (8.40 V pack). A conservative 1C setting for 300 mAh is **0.30 A**, subject to pack instructions. Connect its XT30 main lead and 3-pin balance lead as the charger requires. A 1S USB/TP4056 charger is not compatible. Charge attended on a nonflammable surface.

Run-time rule: use a 2S-compatible per-cell checker/alarm; around 3.5 V/cell under load is a conservative starting alarm. Stop and unplug promptly when it alarms or firmware stops. An alarm is not a cutoff. Remove both the XT30 and any balance-port alarm for storage. A real automatic cutoff requires additional suitable hardware.

Sources, image credits and build files

WEMOS: [S2 Mini photo, board pinout and schematic](#)

TI: [LM2596 buck datasheet](#)

TI: [TPS63070 buck-boost datasheet](#)

TowerPro: [MG90S reference image \(not proof of continuous rotation\)](#)

Diodes: [BS250P terminal drawing](#)

onsemi: [2N3904BU terminal drawing](#)

Battery photo: Lumenier / RaceDayQuads (page 3). Converter and connector photos: user. Third-party images are not MIT-licensed.

What is underneath the deck?

The fuse protects the input wiring; the small perfboard measures battery voltage. Neither is a charger.

F_IN: a compact fuse candidate



Littelfuse 0251004.MXL

PICO II 251 series

4 A, very fast acting

125 V DC rated

300 A DC interrupt rating

Body: 7.11 mm long,

2.80 mm maximum diameter.

Leads and insulation add space.

251-series reference photo

Appearance / markings may vary

[DigiKey: 0251004.MXL / purchase page](#)

[Littelfuse: specifications and mechanical drawing](#)

Why these extra parts are here

Fuse: opens the battery-positive feed during a sufficiently large overcurrent, such as a wiring short. It is one-time use; replace after finding the fault. It is not low-battery protection or a precise 4 A current limiter.

Perfboard: a small soldering board holding the page 4 voltage divider and two-transistor enable circuit. GPIO3 reads scaled battery voltage; GPIO7 enables the reading. This supports the existing firmware monitoring. It carries no servo current.

Capacitors: the nearby 220 uF and 100 nF parts help smooth the 5 V supply. They do not replace an adequately sized converter.

Where the fuse connects

XT30 harness +

F_IN fuse

VBAT_SW: buck IN+ and page 4 sensing feed

Assembly: put the fuse close to the battery connector in the positive harness lead. This axial candidate is soldered inline and insulated with strain relief; it does not require a bulky cartridge holder. Either fuse lead can face the battery. Keep motor current out of the sensing perfboard.

Still provisional: validate 4 A against measured startup current, wire size and fault current. The Blender fuse is a generic placeholder; lead bends, insulation and mounting need a fit check. Photo: Littelfuse / DigiKey, reference image supplied with this product listing.